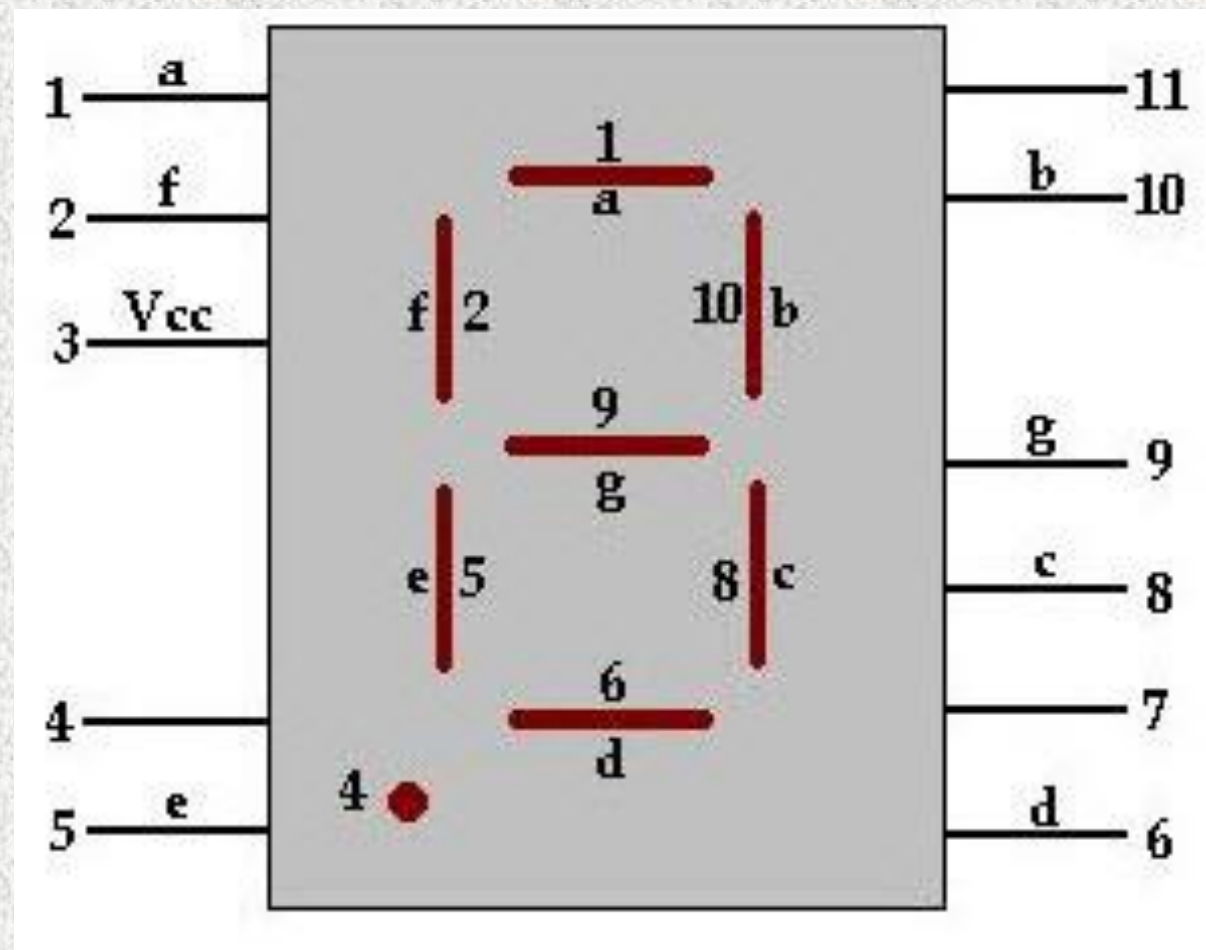


MAR Sensors

Seven Segment
Display



Seven Segment Display

- The seven segment display is the most common display device used in many gadgets, and electronic appliances like digital meters, digital clocks, microwave oven and electric stove, etc.
- These displays consist of seven segments of LEDs assembled into a structure like numeral 8.



- Actually seven segment displays contain about 8-segments wherein an extra 8th segment is used to display dot.
- This segment is useful while displaying non integer number.
- Seven segments are indicated as A-G.
- These segments come in two configurations, they are common cathode and common anode.



Common Cathode Configuration

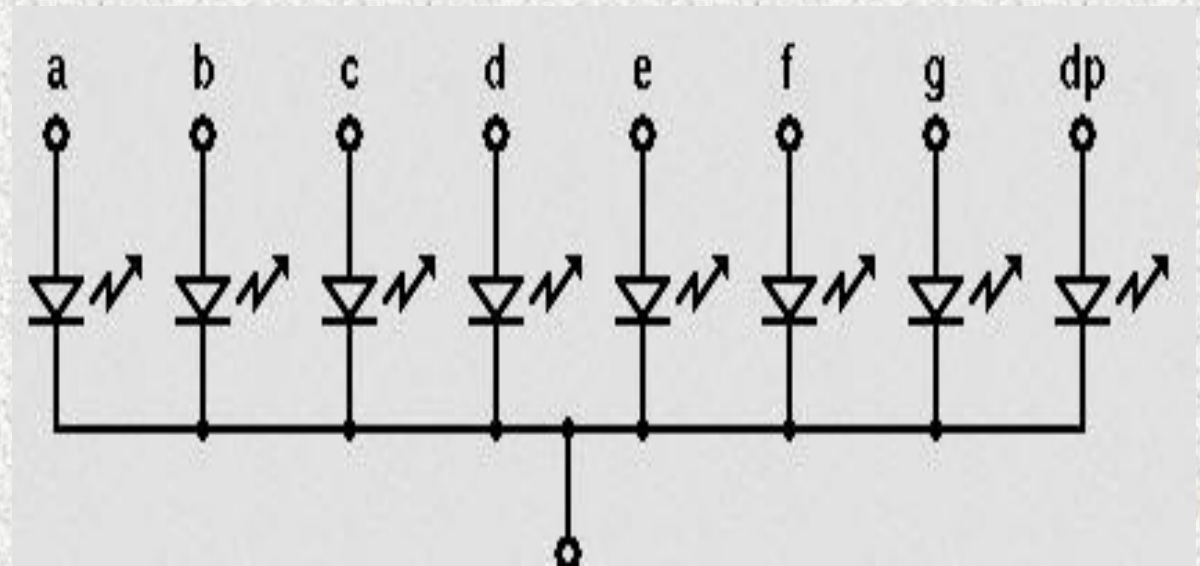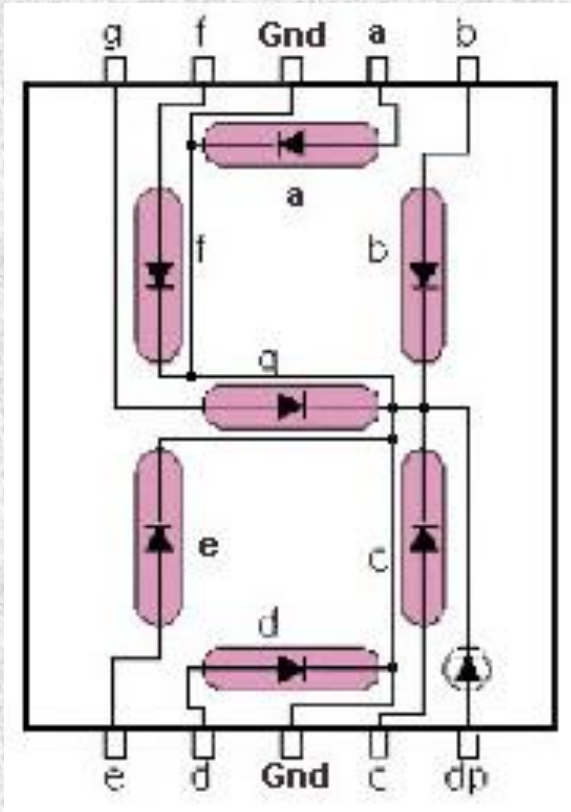

Common Cathode Configuration

- In this type of display, all the cathode connections of the LED segments are connected together to logic 0 or ground.
- The separate segments are lightened by applying the logic 1 or HIGH signal through a current limiting resistor to forward bias the individual anode terminals 'a' to 'g'.

Common Anode Configuration

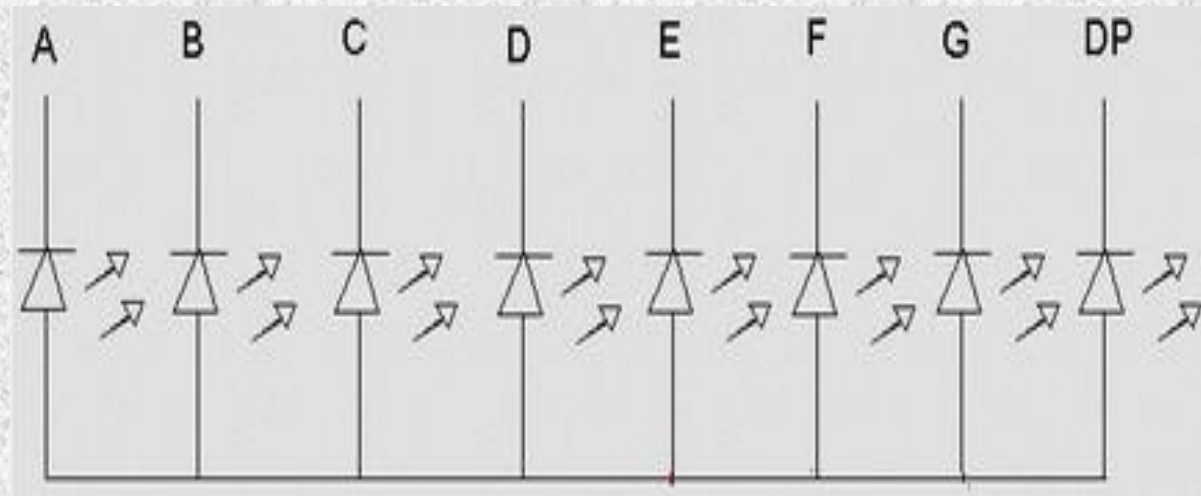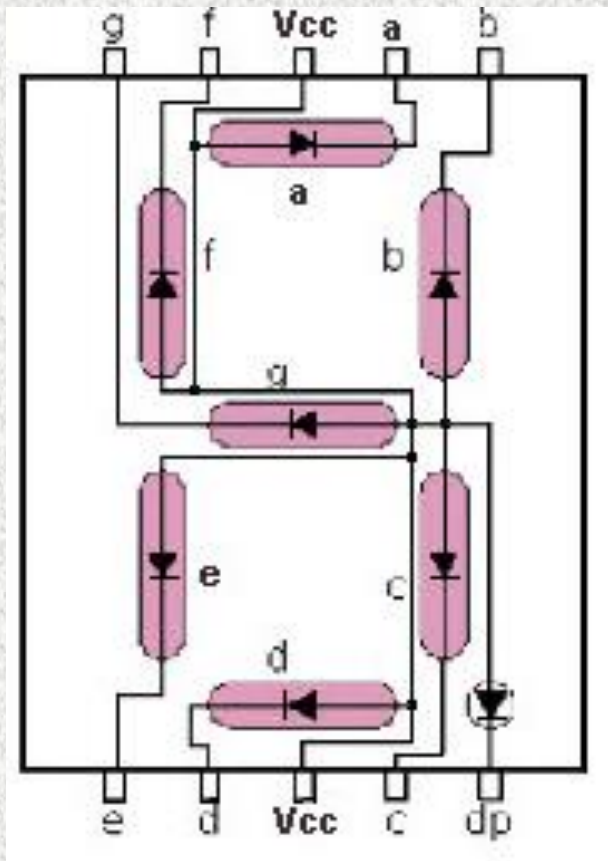

Common Anode Configuration


- In this type of display, all the anode connections of the LED segments are connected together to logic 1.
- The separate segments are lightened by applying of the logic 0 or LOW signal through a current limiting resistor to the cathode of the particular segment a to g.

- Common anode seven segment displays are very popular as many logic circuits can sink more current than they can source.
- These displays are not a direct replacement in a circuit for a common anode display, as it is the same as connecting the LEDs in reverse, and hence the light emission will not take place.
- Depending upon the decimal number displayed, the particular set of LEDs is forward biased.


Working of Seven Segment Display

- When the power is given to all the segments, then the number 8 will be displayed.
- If we disconnect the power for segment G (that means 7) then that will result number 0.
- The circuit of the seven segment display is designed in such a way that the voltage at different pins can be applied at the same time.
- In the same way, we can form the combinations to display numerals from 0 to 9.

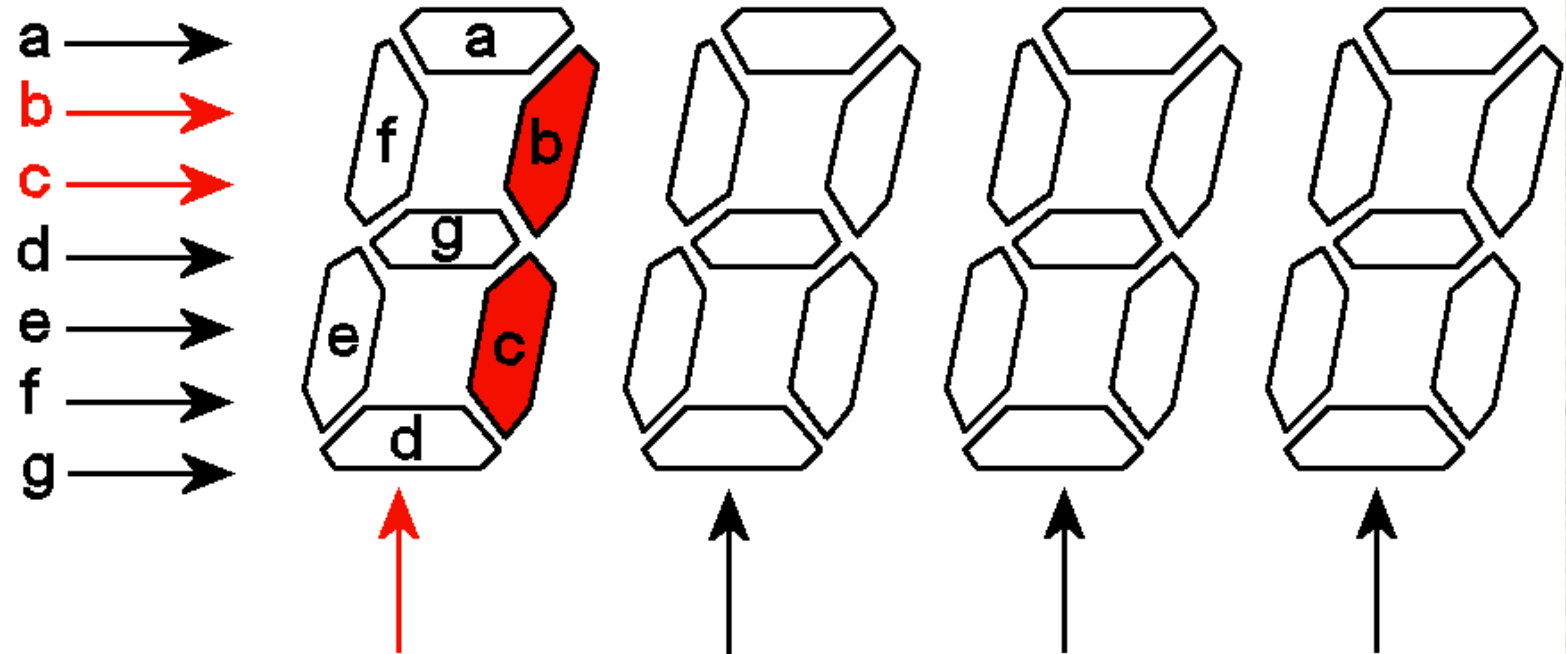- The numeric seven segment displays can also display other characters.
- But generally A-G and L, T, O, S and others are also available. Some problems may occur with the H, X, 2, and Z.
- Generally, the common seven segment display is numeric only. Alphanumeric displays are also available but cost is little more.



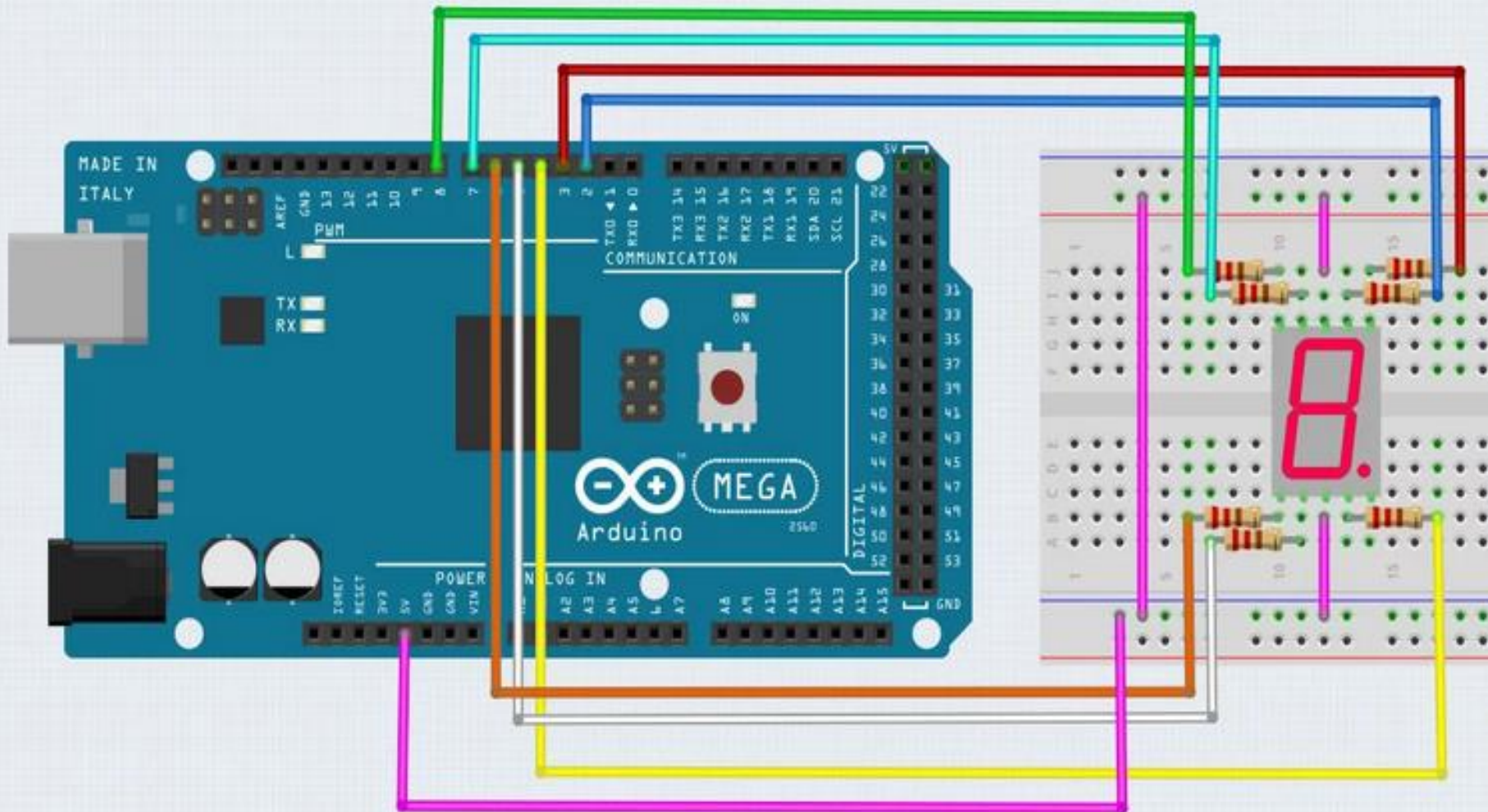Interfacing Seven Segment Display with Arduino



Seven segment pins	Arduino pins	Wire Color
1(e)	6	orange
2(d)	5	white
3,8(COM)	GND	n/a
c	4	yellow
5(dp)	-	
6(b)	3	red
7(a)	2	blue
9(f)	7	cyan
10(g)	8	green

Truth table

Digit	<u>gfedcba</u>	<u>abcdefg</u>	a	b	c	d	e	f	g
0	0×3F	0×7E	on	on	on	on	on	on	off
1	0×06	0×30	off	on	on	off	off	off	off
2	0×5B	0×6D	on	on	off	on	on	off	on
3	0×4F	0×79	on	on	on	on	off	off	on
4	0×66	0×33	off	on	on	off	off	on	on
5	0×6D	0×5B	on	off	on	on	off	on	on
6	0×7D	0×5F	on	off	on	on	on	on	on
7	0×07	0×70	on	on	on	off	off	off	off
8	0×7F	0×7F	on	on	on	on	on	on	on
9	0×6F	0×7B	on	on	on	on	off	on	on
A	0×77	0×77	on	on	on	off	on	on	on
B	0×7C	0×1F	off	off	on	on	on	on	on
C	0×39	0×4E	on	off	off	on	on	on	off
D	0×5E	0×3D	off	on	on	on	on	off	on
E	0×79	0×4F	on	off	off	on	on	on	on
F	0×71	0×47	on	off	off	off	on	on	on

Code for Interfacing

```
void setup()
{
  // define pin modes
  pinMode(2,OUTPUT);
  pinMode(3,OUTPUT);
  pinMode(4,OUTPUT);
  pinMode(5,OUTPUT);
  pinMode(6,OUTPUT);
  pinMode(7,OUTPUT);
  pinMode(8,OUTPUT);
}
```

```
void loop()
{
  // loop to turn leds of seven seg ON
  for(int i=2;i<9;i++) {
    digitalWrite(i,HIGH);
    delay(600);
  }
  // loop to turn leds of seven seg OFF
  for(int i=2;i<9;i++)
  {
    digitalWrite(i,LOW);
    delay(600);
  }
  delay(1000); }
```